

# Laboratory 5:

## AN ENHANCED PROCESSOR

### OBJECTIVES

- The purpose of this lab is to learn how to connect simple input (switches) and output devices (LEDs and 7-segment) to an FPGA chip and implement a circuit that uses these devices.
- Design an enhanced processor based on the simple processor in lab 4.

### PREPARATION FOR LAB 5

- Finish Pre Lab 5 at home.
- Students have to simulate all the exercises in Pre Lab 5 at home. All results (codes, waveform, RTL viewer, ... ) have to be captured and submitted to instructors prior to the lab session.  
*If not, students will not participate in the lab and be considered absent this session.*

### REFERENCE

1. Intel FPGA training



# Laboratory 5:

## AN ENHANCED PROCESSOR

### EXPERIMENT 1

**Objective:** Design and implement a simple processor.

**Requirement:** Design and implement the processor which is shown in Figure 1. Then connect the enhanced processors to a memory and output register (Figure 2).


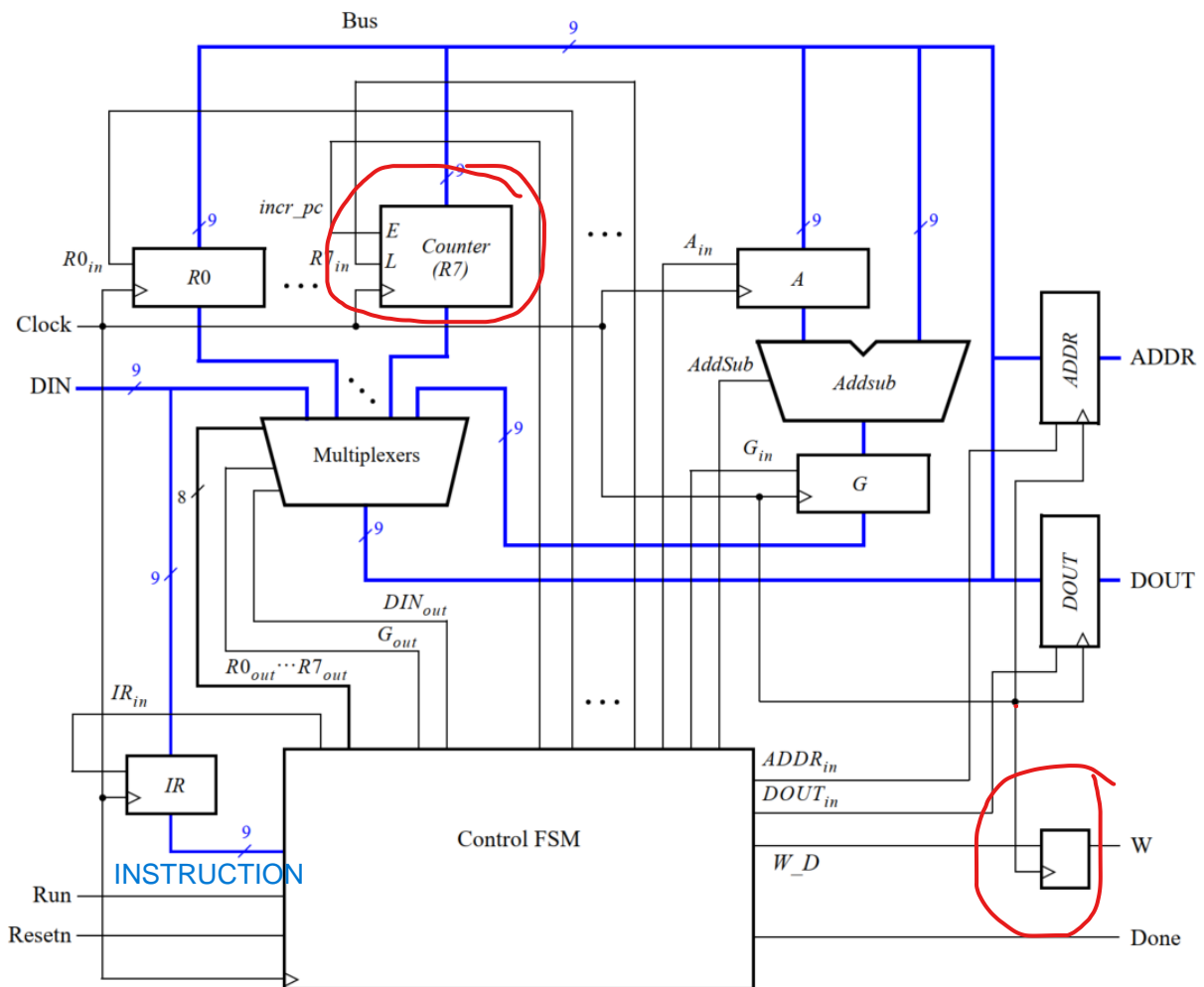


Figure 1: A reference schematic of the enhanced processor.

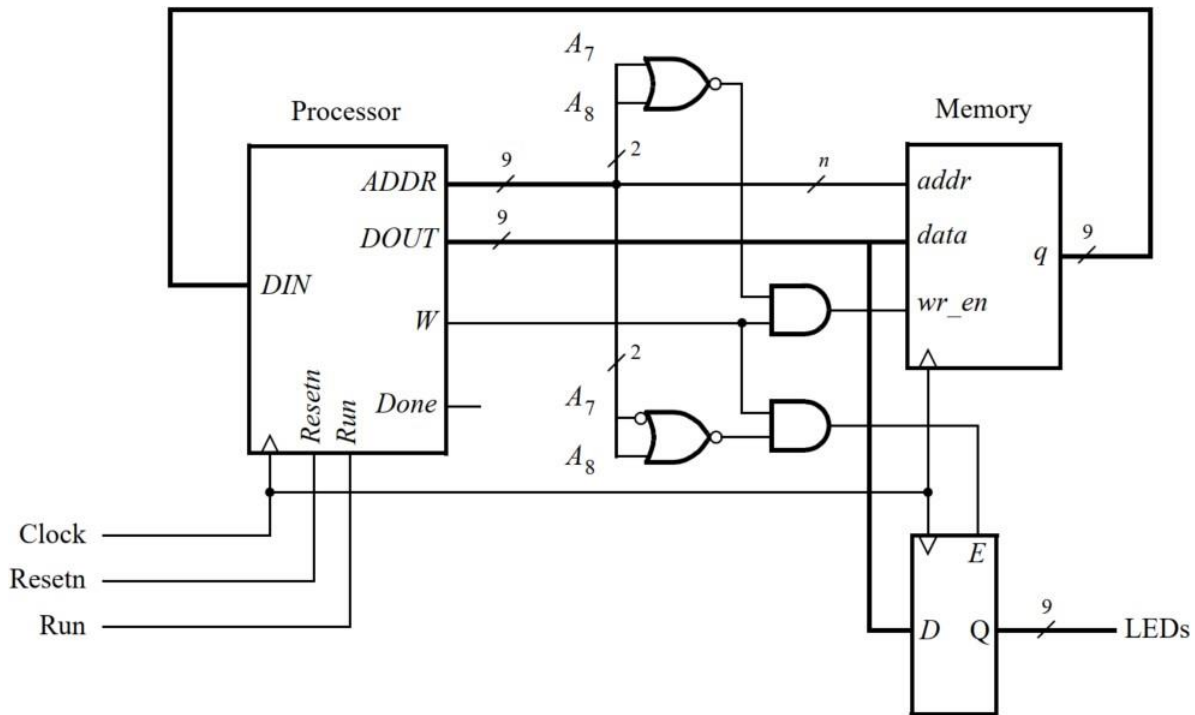

## Laboratory 5: AN ENHANCED PROCESSOR



*Figure 2:* Connecting the enhanced processor to a memory and output register.

### **Instruction:**

- Create a new Quartus project for the enhanced version of the processor.
- Write System Verilog code for the processor and test your circuit by using functional simulation: apply instructions to the DIN port and observe the internal processor signals as the instructions are executed. Pay careful attention to the timing of signals between your processor and external memory; account for the fact that the memory has registered input ports, as we discussed for Figure 2.
- Create another Quartus project that instantiates the processor, memory module, and register shown in Figure 2. Use the Quartus IP Catalog to create the RAM: 1-PART memory module. Follow the instructions provided by the wizard to create a memory that has one 9-bit wide read/write data port and is 128 words deep. Ensure that the output is not registered. Use a MIF file to store instructions in the memory that are to be executed by your processor. An example program in the form of a MIF file is shown in Figure 3. This program display an 8-bit counter value on the

# Laboratory 5:

## AN ENHANCED PROCESSOR

LEDs output port. Loops are used in the program to create delays so that the counter values are not changed too quickly to be observed. Comments are included in the MIF file in Figure 3 to describe the program's code.

```

DEPTH = 128;
WIDTH = 9;
ADDRESS_RADIX = HEX;
DATA_RADIX = BIN;
CONTENT
BEGIN

% This code displays a count (in register R2) on the red LEDs.
00 : 001001000; %      mvi    R1,#1           // initialize R
01 : 000000001;
02 : 001010000; %      mvi    R2,#0           // counter to display on LEDs
03 : 000000000;
04 : 001011000; % Loop  mvi    R3,#010000000    // R3 = address of LEDs register
05 : 010000000;
06 : 101010011; %      st     R2,R3           // write to LEDs
07 : 010010001; %      add    R2,R1           // increment counter for LEDs
08 : 001011000; %      mvi    R3,#111111111    // delay value
09 : 111111111;
0A : 000101111; %      mv     R5,R7           // save address of next inst.
0B : 001100000; % Outer  mvi    R4,#111111111    // nested delay loop
0C : 111111111;
0D : 000000111; %      mv     R0,R7           // save address of next inst.
0E : 011100001; % Inner  sub    R4,R1           // decrement loop delay variable
0F : 110111000; %      mvnz   R7,R0           // continue Inner loop if R4 !=0
10 : 011011001; %      sub    R3,R1           // decrement outer loop delay
11 : 110111101; %      mvnz   R7,R5           // continue Outer loop if R3 !=0
12 : 001111000; %      mvi    R7,#Loop        // execute again
13 : 000000100;

END;
```

➤ Figure 3: An example program in a memory initialization file (MIF).

➤ Use functional simulation to test the circuit. Ensure that data is read properly from the memory and executed by the processor

➤ Include in your project the necessary pin assignments to implement your circuit on your DE-series board. Use switch SW9 to drive the processor's Run input, use KEY0 for Resetn, and



# Laboratory 5:

## AN ENHANCED PROCESSOR

use the board's 50 MHz clock signal as the Clock input. Since the circuit needs to run properly at 50 MHz, make sure that a timing constraint is set in Quartus to constrain the circuit's clock to this frequency. Read the Report produced by the Quartus Timing Analyzer to ensure that your circuit operates at this speed; if not, use the Quartus tools to analyze your circuit and modify your Verilog code to make a more efficient design that meets the 50-MHz speed requirement. Also note that the Run input is asynchronous to the clock signal, so make sure to synchronize this input using flip-flops. Connect the LEDs register in Figure 2 to LEDR8–0 so that you can observe the output produced by the processor.

➤ Compile the circuit, download it into the FPGA chip, and ensure that your program runs properly.

**Check:** Your report has to show two results:

**The Code:**

### **module Processor(**

```

    input logic [8:0] DIN,
    input clk,
    input logic Run, Resetn,
    output logic [8:0] ADDRout, DOUTout,
    output logic Done, Win,
    output [8:0] IR_test, BUS_test
);
reg [8:0] IRout, R0d, R1d, R2d, R3d, R4d, R5d, R6d, R7d, Ad, hehe, hehed;
logic incr_pc, ADDRin, DOUTin, W_D;
reg [7:0] Rout, Rin;
logic [8:0] Bus;
//assign Zero = G_Q == 0;
reg IRin, Ain, Addsub, Gin, Gout, DINout, incre_PC, Zero;
ControlUnitFSM ControlunitFSM(.Clk(clk), .Run(Run), .Resetn(Resetn), .Zero(Zero),
    .IR(IR_Q), .IRin(IRin), .Rout(Rout), .Gout(Gout), .DINout(DINout),
    .Rin(Rin), .Ain(Ain), .Gin(Gin), .AddSub(AddSub), .incr_pc(incr_pc),
    .ADDRin(ADDRin), .DOUTin(DOUTin), .W(W_D), .Done(Done));

NineBitRegister IR(.clk(clk), .Enable(IRin), .D(DIN), .Q(IRout));
OneBitRegister ff_W(.clk(clk), .R(W_D), .Q(Win));
NineBitRegister R0(.clk(clk), .Enable(Rin[0]), .D(Bus), .Q(R0d));
NineBitRegister R1(.clk(clk), .Enable(Rin[1]), .D(Bus), .Q(R1d));
NineBitRegister R2(.clk(clk), .Enable(Rin[2]), .D(Bus), .Q(R2d));
NineBitRegister R3(.clk(clk), .Enable(Rin[3]), .D(Bus), .Q(R3d));
NineBitRegister R4(.clk(clk), .Enable(Rin[4]), .D(Bus), .Q(R4d));
NineBitRegister R5(.clk(clk), .Enable(Rin[5]), .D(Bus), .Q(R5d));
NineBitRegister R6(.clk(clk), .Enable(Rin[6]), .D(Bus), .Q(R6d));

```



# Laboratory 5:

## AN ENHANCED PROCESSOR

```

NineBitRegister2 R7(.clk(clk),.enable(Rin[7]),.incr_pc(incr_pc),.Resetn(Resetn),.D(Bus),.Q(R7d));
NineBitRegister A(.clk(clk),.Enable(Ain),.D(Bus),.Q(Ad));
NineBitRegister G(.clk(clk),.Enable(Gin),.D(hehe),.Q(hehed),.Zero(Zero));
//NineBitRegister ADDR(.clk(clk),.Enable(ADDRin),.D(Bus),.Q(ADDRout));
//NineBitRegister DOUT(.clk(clk),.Enable(DOUTin),.D(Bus),.Q(DOUTout));
Multiplexer
Multiplexer(.DINout(DINout),.Gout(Gout),.Rout(Rout),.DIN(DIN),.R0(R0d),.R1(R1d),.R2(R2d),.R3(R3d),.
R4(R4d),.R5(R5d),.R6(R6d),.R7(R7d),.G(hehed),.Bus(Bus));
AddSub AddSub(.A(Ad),.B(Bus),.AddSub(Addsub),.G(hehe));
NineBitRegister2 ff_ADDR(.clk(clk),.enable(ADDRin),.D(Bus),.Q(ADDRout));
NineBitRegister2 ff_DOUT(.clk(clk),.enable(DOUTin),.D(Bus),.Q(DOUTout));

```

```

assign IR_test = IRout;
assign BUS_test = Bus;
endmodule

```

### module ControlUnitFSM(

```

input Resetn, Clk, Run,
input [8:0] IR,
input Zero,
output [7:0] Rout,
output DINout, Gout,
output IRin, Ain, Gin, AddSub,
output incr_pc, ADDRin, DOUTin, W,
output [7:0] Rin,
output Done
);

logic [2:0] Tstep_Q, Tstep_D;
logic [2:0] III, XXX, YYY;
logic [7:0] RXin_temp, RXout_temp, RYout_temp;

```

```

assign III = IR[8:6];
assign XXX = IR[5:3];
assign YYY = IR[2:0];

```

```

decoder rxin(.in(XXX),.register(RXin_temp));
decoder rxout(.in(XXX),.register(RXout_temp));
decoder ryout(.in(YYY),.register(RYout_temp));

```

```

parameter T0 = 3'b000, T1 = 3'b001, T2 = 3'b010, T3 = 3'b011, T4 = 3'b100, T5 = 3'b101;

```

```

// Control FSM state table
always @(Tstep_Q, Run, Done)
case (Tstep_Q)
T0: // instruction fetch
if (~Run) Tstep_D = T0;

```



# Laboratory 5:

## AN ENHANCED PROCESSOR

```

    else Tstep_D = T1;
T1: // wait cycle for synchronous memory
    Tstep_D = T2;
T2: // this time step stores the instruction word in IR
    Tstep_D = T3;
T3: // some instructions end after this time step
    if (Done) Tstep_D = T0;
    else Tstep_D = T4;
T4: // always go to T5 after this
    Tstep_D = T5;
T5: // instructions end after this time step
    Tstep_D = T0;
default: Tstep_D = 3'bxxx;
endcase

```

parameter mv = 3'b000, mvi = 3'b001, add = 3'b010, sub = 3'b011, ld = 3'b100, st = 3'b101, mvnz = 3'b110;

```

// Control FSM outputs
always @(*) begin
Done = 1'b0; Ain = 1'b0; Gin = 1'b0; AddSub = 1'b0; IRin = 1'b0; Rin = 8'b0;
DINout = 1'b0; Gout = 1'b0; Rout = 8'b0;
incr_pc = 1'b0; ADDRin = 1'b0; DOUTin = 1'b0; W = 1'b0;
    case (Tstep_Q)
T0: begin // fetch the instruction
        Rout = 8'b10000000; // put pc onto the internal bus
        ADDRin = 1'b1;
        incr_pc = Run; // to increment pc
    end
T1: // wait cycle for synchronous memory
        ;

        T2: // store instruction on DIN in IR
            IRin = 1'b1;
T3: // define signals in T3
    case (III)
        mv: begin
            Rout = RYout_temp;

            Rin = RXin_temp;
            Done = 1'b1;

        end
        mvi: begin

            Rout = 8'b10000000;
            ADDRin = 1'b1;
            incr_pc = 1'b1;

        end
        add, sub: begin
            Rout = RXout_temp;

            Ain = 1'b1;
        end
    endcase
end

```



# Laboratory 5:

## AN ENHANCED PROCESSOR

```

end
ld, st: begin
Rout = RYout_temp;
ADDRin = 1'b1;
end
mvnz: begin
if (Zero) begin
Rout = RYout_temp;
Rin = RXin_temp;
Done = 1'b1;
end
else
Done = 1'b1;
end
default: begin
Done = 1'b0; Ain = 1'b0; Gin = 1'b0;
AddSub = 1'b0; IRin = 1'b0; Rin = 8'b0;
DINout = 1'b0; Gout = 1'b0; Rout = 8'b0;
incr_pc = 1'b0; ADDRin = 1'b0; DOUTin = 1'b0; W = 1'b0;
end
endcase
T4: // define signals T4
case (III)
add: begin
Rout = RYout_temp;
Gin = 1'b1;
end
sub: begin
Rout = RYout_temp;
Gin = 1'b1;
AddSub = 1'b1;
end
end

mvi: // wait cycle for synchronous memory
;
ld: // wait cycle for synchronous memory
;
st: begin
Rout = RXout_temp;
DOUTin = 1'b1;
W = 1'b1;
end
default: begin
Done = 1'b0; Ain = 1'b0;
AddSub = 1'b0; IRin =
1'b0; Rin = 8'b0;

```





# Laboratory 5:

## AN ENHANCED PROCESSOR

```

1'b0; Rout = 8'b0;
1'b0; DOUTin = 1'b0; W = 1'b0;

    endcase
T5: // define T5
    case (III)
        add, sub: begin
            Gout = 1'b1;

        end

        mvi: begin
            Rin = RXin_temp;
            Done = 1'b1;

        end

        ld: begin
            DINout = 1'b1;

            Rin = RXin_temp;
            Done = 1'b1;

        end

        st: // wait cycle for synhronous memory
            Done = 1'b1;
        default: begin

        end

    end
    Gin = 1'b0;
    1'b0; Rin = 8'b0;
    1'b0; Rout = 8'b0;
    1'b0; DOUTin = 1'b0; W = 1'b0;

    endcase
endcase
end

// Control FSM flip-flops
always @(posedge Clk, negedge Resetn)
    if (!Resetn)
        Tstep_Q <= T0;
    else
        Tstep_Q <= Tstep_D;
endmodule
DINout = 1'b0; Gout =
incr_pc = 1'b0; ADDRin =
end
Done = 1'b0; Ain = 1'b0;
AddSub = 1'b0; IRin =
DINout = 1'b0; Gout =
incr_pc = 1'b0; ADDRin =
end

```



# Laboratory 5:

## AN ENHANCED PROCESSOR

```
module decoder(
    input logic [2:0] in,
    output logic [7:0] register
);
always_comb begin
    case (in)
        3'b000: register = 8'b00000001;
        3'b001: register = 8'b00000010;
        3'b010: register = 8'b00000100;
        3'b011: register = 8'b00001000;
        3'b100: register = 8'b00010000;
        3'b101: register = 8'b00100000;
        3'b110: register = 8'b01000000;
        3'b111: register = 8'b10000000;
    endcase
end
endmodule
```

```
module AddSub(
    input logic [8:0] A,B,
    input logic [0:0] AddSub,
    output logic [8:0] G
);
always_comb begin
    case (AddSub)
        1: G=A+B;
        default: G= A-B;
    endcase
end
endmodule
```

```
module logicgates(
    input logic [8:0] ADDRin,DOUTin,
    input logic W,
    output logic wr_en,Enable,
    output logic [6:0] ADDR,
    output logic [8:0] DOUT
);
assign ADDR = ADDRin[6:0];
reg NOR1,NNOR1;
assign NOR1 = ~(ADDRin[7]|ADDRin[8]);
assign wr_en = NOR1 & W;// if 1 => wr_en on
assign NNOR1 = (~(~ADDRin[7])|ADDRin[8]);
assign Enable = NNOR1&W;
assign DOUT =DOUTin;
endmodule
```



# Laboratory 5:

## AN ENHANCED PROCESSOR

### module Multiplexer(

```
input [8:0] DIN,  
input [8:0] R0, R1, R2, R3, R4, R5, R6, R7,  
input [8:0] G,  
input [7:0] Rout,  
input DINout, Gout,  
output [8:0] Bus  
);
```

```
logic [9:0] Sel;
```

```
assign Sel = {Rout, DINout, Gout};
```

```
always_comb begin
```

```
    case (Sel)
```

```
        10'b1000000000: Bus = R7;  
        10'b0100000000: Bus = R6;  
        10'b0010000000: Bus = R5;  
        10'b0001000000: Bus = R4;  
        10'b0000100000: Bus = R3;  
        10'b0000010000: Bus = R2;  
        10'b0000001000: Bus = R1;  
        10'b0000000100: Bus = R0;  
        10'b0000000010: Bus = DIN;  
        10'b0000000001: Bus = G;  
        default: Bus = '0;
```

```
    endcase
```

```
end
```

```
endmodule
```

### module NineBitRegister(

```
    input logic[0:0] Enable,  
    input clk,  
    input logic [8:0] D,  
    output logic [8:0] Q,  
    output logic Zero
```

```
);
```

```
always@(posedge clk) begin
```

```
    if ( Enable) begin
```

```
        Q<=D;
```

```
        //Q=D;
```

```
    end
```

```
end
```

```
always@(posedge clk) begin
```

```
    if (D==0) begin
```



# Laboratory 5:

## AN ENHANCED PROCESSOR

```
Zero = 1;  
end  
else  
begin  
Zero = 0;  
end  
end  
endmodule
```

### **module NineBitRegister2(**

```
input clk, enable, incr_pc, Resetn,  
input [8:0] D,  
output [8:0] Q  
);  
always@(posedge clk) begin  
    if (!Resetn)  
        Q <= 9'b0;  
    else if (enable)  
        Q <= D;  
    else if (incr_pc)  
        Q <= Q + 1'b1;  
end  
endmodule
```

### **module OneBitRegister(**

```
input clk,  
input R,  
output Q  
);  
always@(posedge clk) begin  
    Q <= R;  
end  
endmodule
```

### **module counter(**

```
input logic CLK,RST,  
output logic [4:0] ADDRESS  
);  
always@(posedge CLK, negedge RST) begin  
    if(!RST) begin  
        ADDRESS = 0;  
    end  
    else begin  
        ADDRESS = ADDRESS +1;  
    end  
end
```



# Laboratory 5:

## AN ENHANCED PROCESSOR

```
end  
endmodule
```

```
module W(  
    input logic D,  
    input logic clk,  
    output logic Q  
);  
always@(posedge clk) begin  
    Q=D;  
end  
endmodule
```

```
module MyROM(  
    input logic [6:0] addr,  
    input logic [8:0] data,  
    input logic wr_en,  
    input logic clk,  
    output logic [8:0] q  
);  
  
logic [8:0] memory [0:127]; // 128 words of 9-bit memory  
  
initial begin  
    $readmemb("hehe.txt",memory);  
end  
  
always_ff @ (posedge clk) begin  
    if (wr_en) begin  
        memory[addr] <= data;  
    end  
    q = memory[addr];  
end  
  
endmodule
```

### **file hehe.txt (file data ROM)**

```
001010000  
010011000  
101010110  
001000001  
001000000  
001010000  
010011000
```




# Laboratory 5:

## AN ENHANCED PROCESSOR


101110010  
001000001  
001011000  
111111111  
000101111

- The waveform to prove the circuit works correctly.

- Waveform processor

 

- Waveform full:

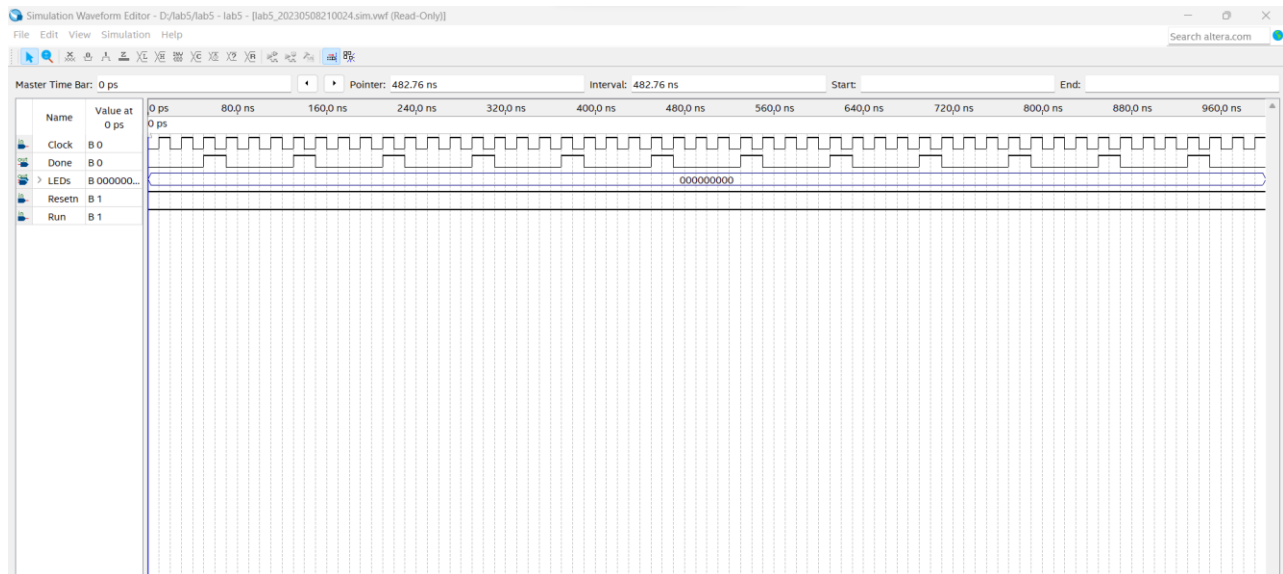

- The result of RTL viewer.



# Laboratory 5: AN ENHANCED PROCESSOR

